

Assignment Project Exam Help

# CPU Datapaths 1

<https://tutorcs.com>

CS 154: Computer Architecture

WeChat: [tutorcs](#)

Winter 2020

Ziad Matni, Ph.D.

Dept. of Computer Science, UCSB

# Administrative

---

- Exam grades will be announced by the weekend

Assignment Project Exam Help

<https://tutorcs.com>

- New lab this week (Lab 6)

WeChat: cstutorcs

# Lecture Outline

---

- Logic Design Refresher

- Datapaths


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs
 
# General (and Simplified) CPU Hardware Design

*REMEMBER: This is drawn in abstract blocks, NOT in the exact way the logic hardware actually is!!*



# Information Encoding

- At the very basic level, an electronic logic circuit has:


- Input(s) *deal with logic levels of “0” and “1”*
- Output(s) *and nothing else*
- Power Supply *it's how the circuits actually work*

<https://tutorcs.com>

- Power supply (i.e. a battery) voltage range allows for 2 distinct “levels” within that range

- Low voltage  $\equiv$  Logic **0**
- High voltage  $\equiv$  Logic **1**

 - One wire per bit
- Multi-bit data encoded on multi-wire “**buses**”



# The 2 Types of Logic Building Blocks

- **Combinatorial Logic**

- Output is a direct “result” of a combination of inputs
- Input changes mean output changes *immediately*\*

Assignment Project Exam Help

<https://tutorcs.com>

- **Sequential Logic**


- Output can *optionally* \*\* remain unchanged
- It means that this kind of logic can keep an old output the same *even if the input(s) change(s)!*
- In other words, these circuits have “memory” of “old states”

WeChat: cstutorcs

\* In the **physical world**, there is no such thing as “change occurring immediately”.  
The use of this term here just means “practically immediately”.

\*\* This means the output must rely on a “special” input to **enable** the output to change.





 
# Graphical Symbols of Basic Combinatorial Logic Elements



Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs

     

 
# Multiplexers (Muxes)

- Combinatorial circuits who function as a “chooser” between multiple inputs to be “driven to” the output
- Always multiple inputs (N), always ONE output (N to-1 mux)
  - Can be drawn symbolically in 2 ways (trapezoid vs oval)  
--- there's NO difference, just a preference in drawing



- 1 of the input data lines gets selected to become the output, based on a 3<sup>rd</sup> “select” (sel) input

 - If **sel** = 0, then  $I_0$  gets to be the output
- If **sel** = 1, then  $I_1$  gets to be the output
- So: **OUTPUT** =  $I_1 \cdot \text{sel} + I_0 \cdot \overline{\text{sel}}$



- The opposite of a Mux is called a **Demultiplexer** (or **Demux**)





# ALUs and Adders

- Combinatorial logic

- ALU takes 2 bus (i.e. multi-bit) inputs and outputs 1 bus, depending on what function (F) is chosen
  - $Y = F(A, B)$


WeChat: cstutorcs

  - Adder is really a sub-set of any ALU – we sometimes want to symbolize it separately
  - $Y = A \text{ bit-add } B \text{ (i.e. } A + B)$


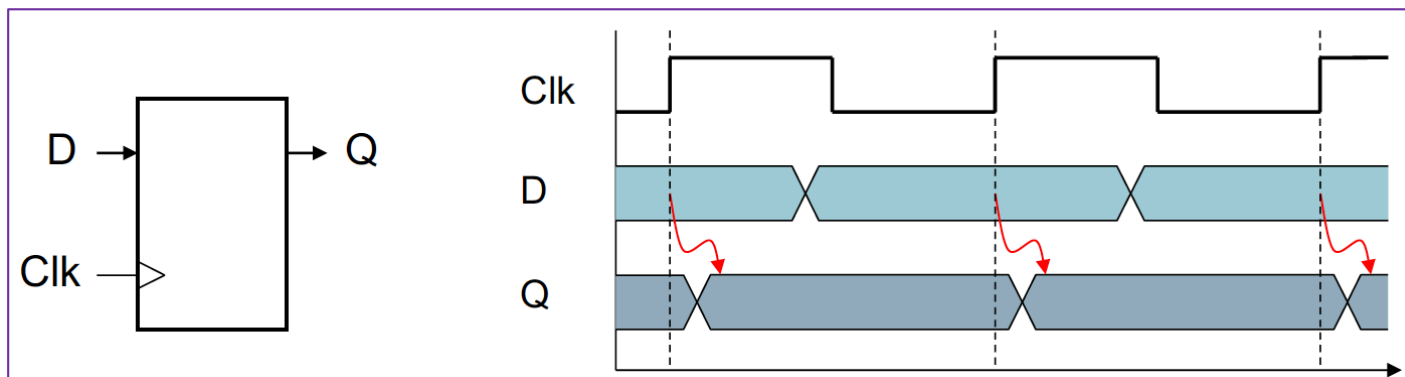
# Registers

- Sequential Logic
- Input passes on to the output ONLY if enabled
  - Otherwise, the output remains in its “old” state
- Typically, registers are D-Flip-Flop circuits
  - Uses a **clock signal** to determine when to update the stored value
  - **Edge-triggered**: update when clock signal changes from 0 to 1



# Registers with Write Control


- Sometimes registers have an additional enabling mechanism: a WRITE-ENABLE input

Assignment Project Exam Help

- Only updates on clock edge when write-enable control input is 1

<https://tutorcs.com>

 - Useful if we don't need to write something right away
  - You can't "mute" the clock signal because it is a global one
  - WRITE-ENABLE is a local signal only to *that particular* register



# Clocking Methodology

- The same clock signal is propagating to multiple parts of the CPU

- Combinational logic transforms data during clock cycles



- i.e. *between* clock edges

- Input from state elements, output to state element

<https://tutorcs.com>  
WeChat: cstutorcs

- Longest delay determines clock period

  - Or better said: clock period determines how long the longest delay can be



# Building a Datapath

---

- **Datapath:** Elements that process data and addresses in the CPU


- Example: Registers, ALUs, muxes, memories, ...


<https://tutorcs.com>

- We will build a MIPS datapath incrementally
  - Refine the overview “simple” design
 
# Simplified CPU Design

*REMEMBER: This is drawn in abstract blocks, NOT in the exact way the logic hardware actually is!!*



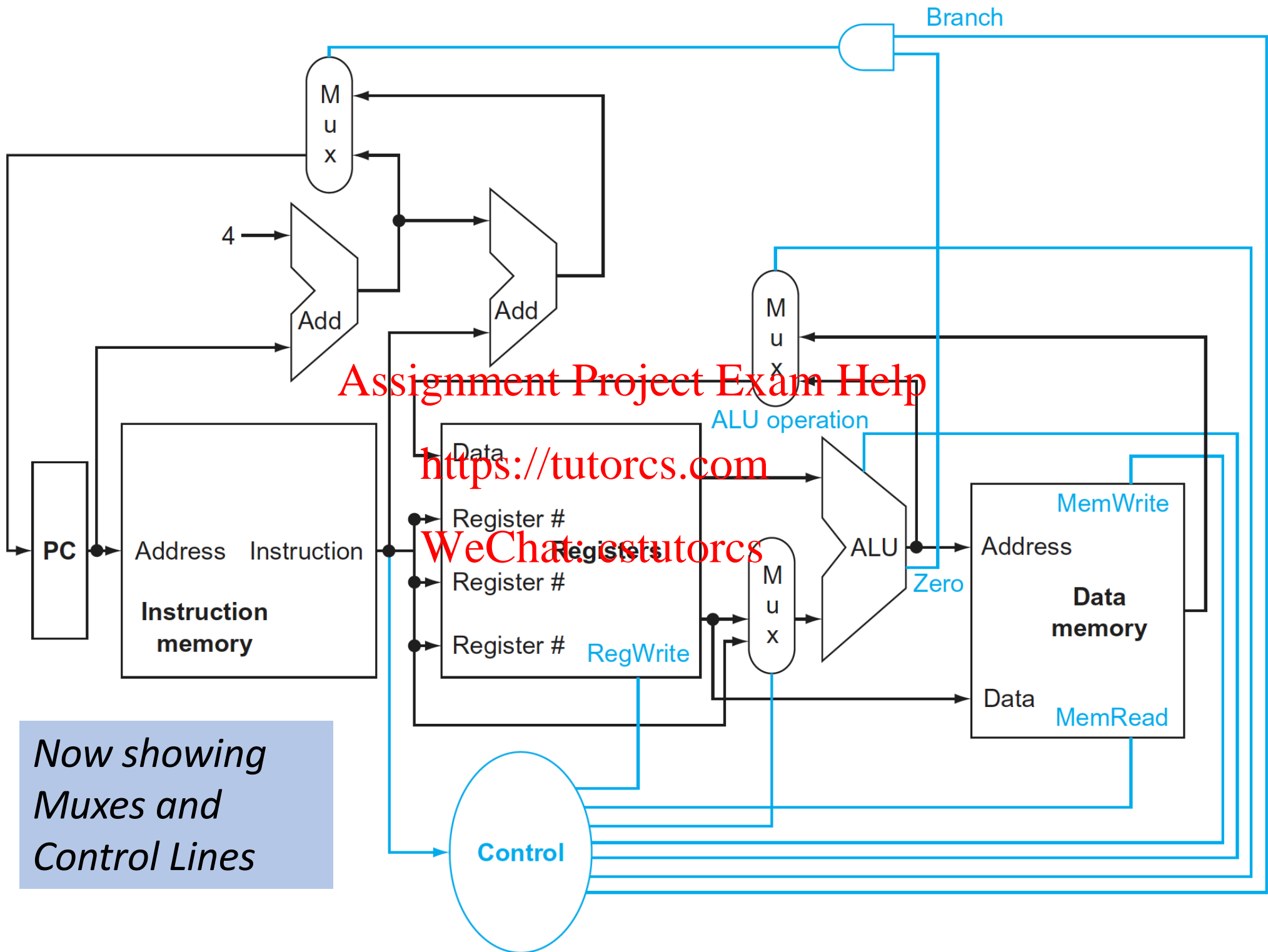

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: estutorcs

Ok...

---

Let's Review it


One Assignment Project Exam Help  
Instruction Type at a Time...

<https://tutorcs.com>

WeChat: cstutorcs



# First: The Instruction Fetch

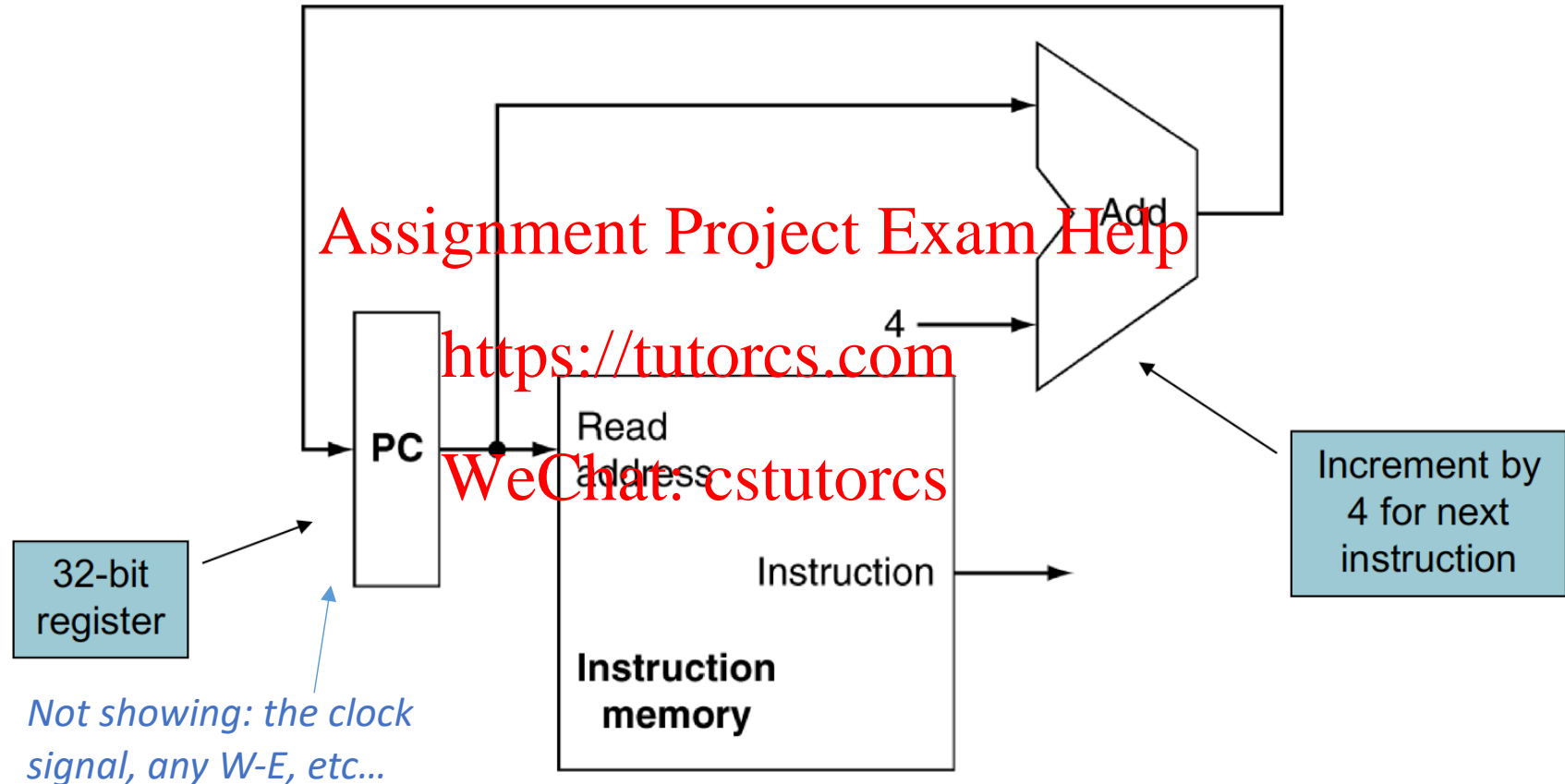

1. To execute **any** instruction, we must start by fetching the instruction from memory.
2. To prepare for executing the *next* instruction, we must also increment the PC so that it points at the next instruction, 4 bytes later.

# R-Format Instructions: 3 Steps


- Read **two** register operands (\$rs, \$rt)
- Perform arithmetic/logical operation
- Write register result (\$rd)

*includes add, sub, and, or, slt  
e.g.: add \$t1, \$t2, \$t3*


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

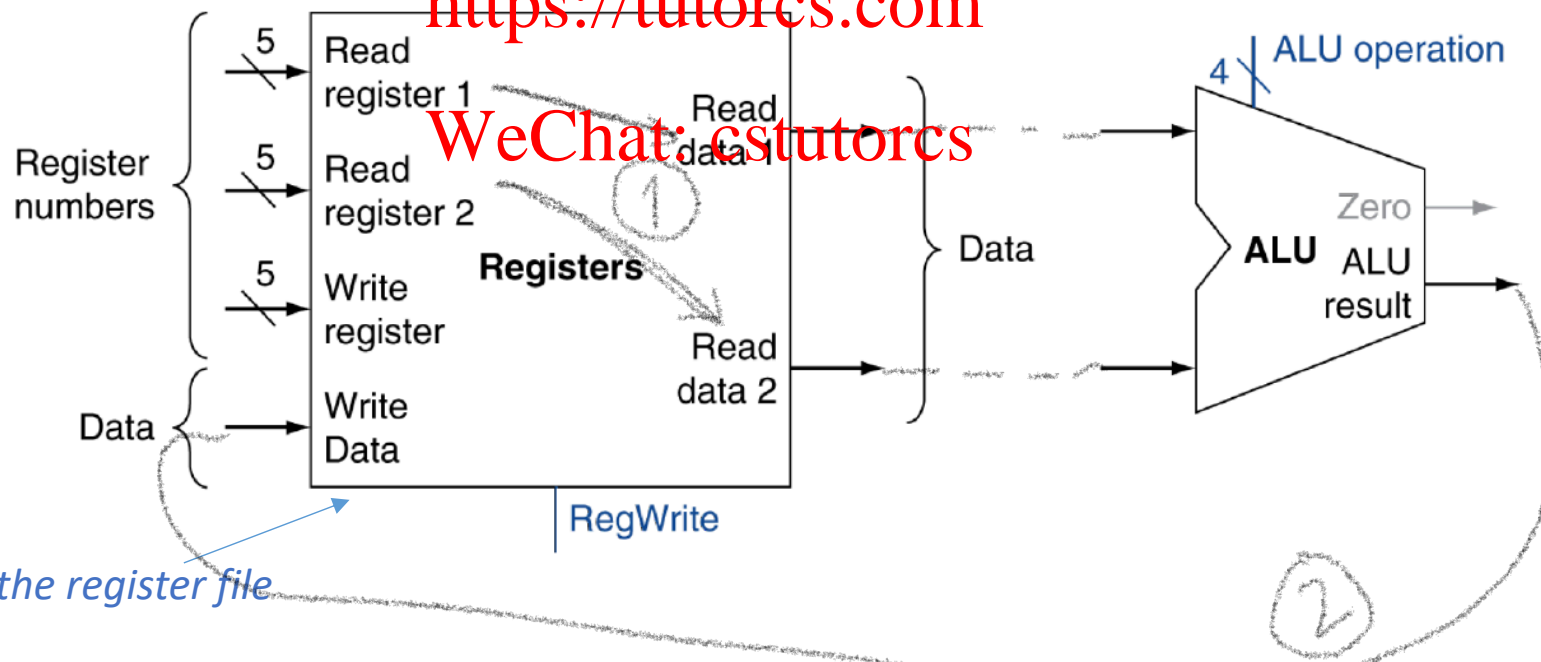


# Register File Read and Write

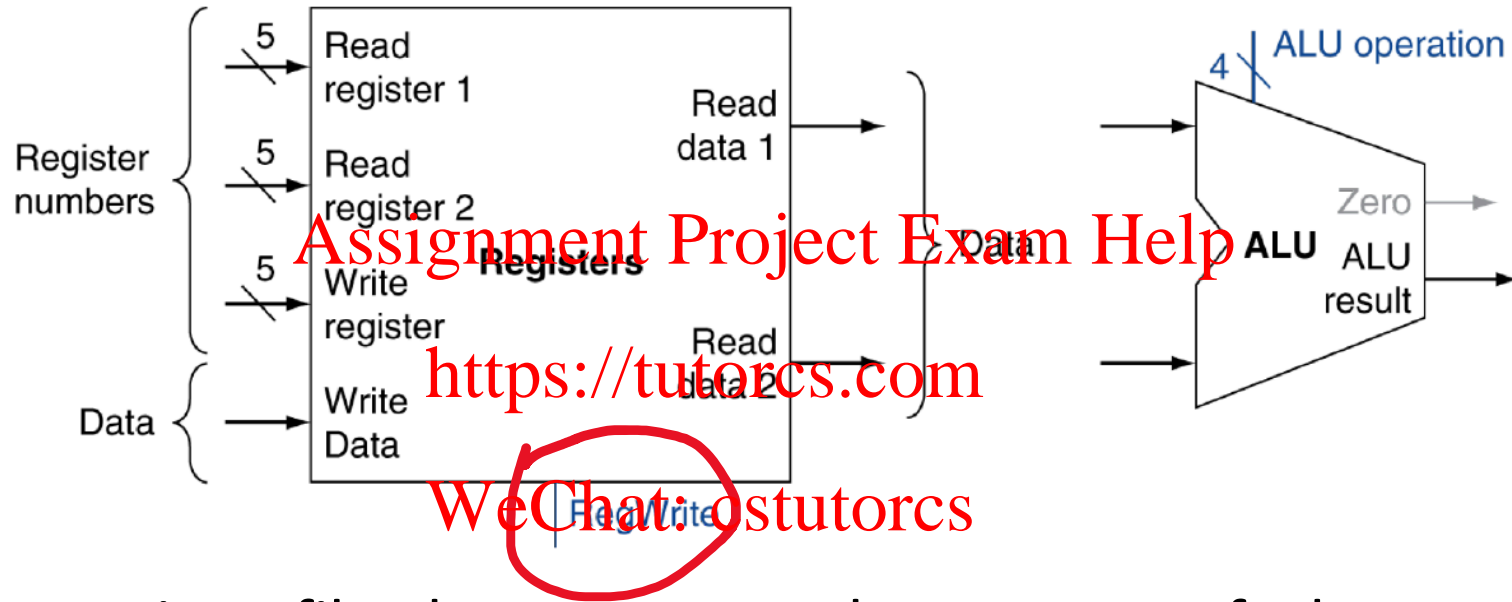

- The register file always outputs the contents of whatever register numbers are on the Read register inputs.
- Writes are controlled by the write control signal, which must be *asserted* for a write to occur at the clock edge.

# The ALU Operation

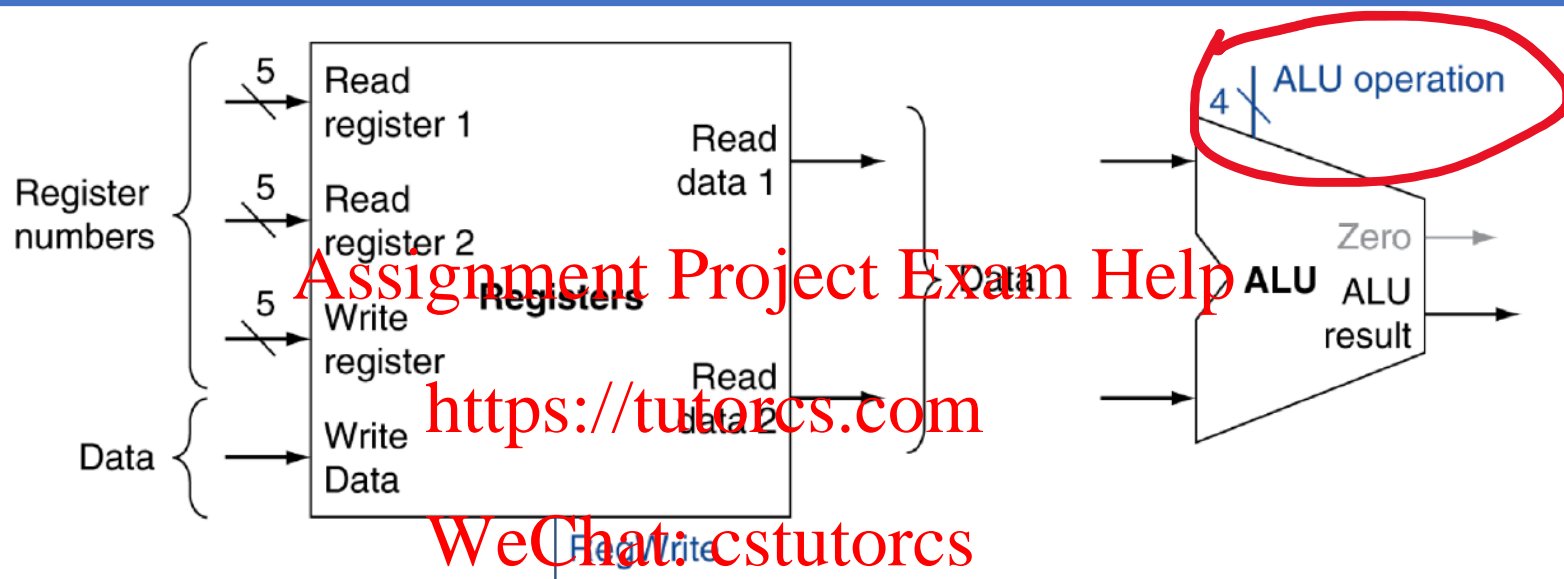

- The ALU takes two 32-bit inputs and produces a 32-bit result
- Also produces a 1-bit signal if the result is 0.
- The 4-bit control signal of the ALU (“ALU operation”) tells it what op it’s performing on the inputs
  - It’s a decoded set of bits... more on those later

# Load/Store Instructions

- Read register operands
- Calculate address using 16-bit offset (immediate)
  - First take the offset and sign-extend it to 32-bits
  - Then use ALU
- Load: Read memory and update register
- Store: Write register value to memory


*includes lw, sw  
e.g.: `Lw $t0, 4($sp)`*

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs

*We'll also need...*

 

a. Data memory unit

 

b. Sign extension unit

# Branch Instructions

includes beq, bne  
e.g.: beq \$t1, \$t2, Label


- Read register operands

- Compare operands

- Use ALU, subtract and check Zero output

- Calculate target address

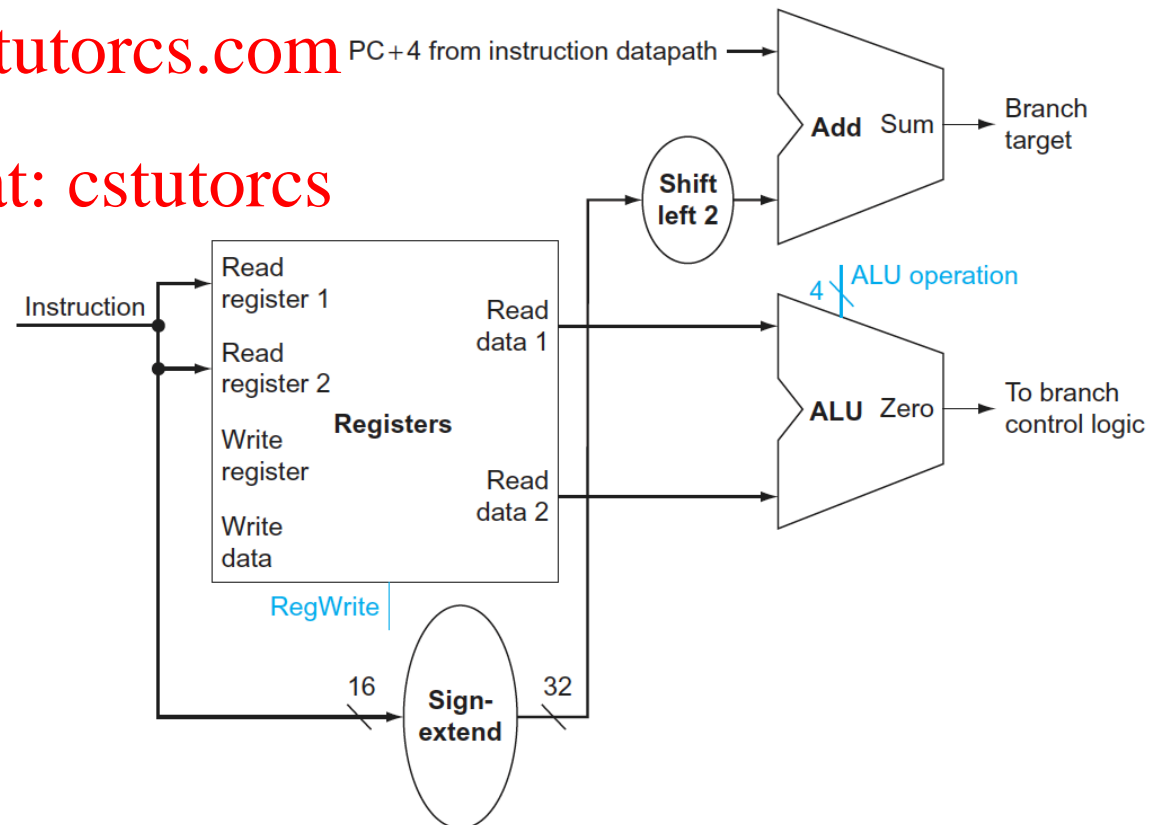- Sign-extend displacement
  - Shift left 2 places
  - Add to PC + 4  
(already calculated by instruction fetch)



# Next Time... Putting them all Together

---

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

# YOUR TO-DOs for the Week

---

- Lab 6 will be up soon...
- Assembly programming assignment

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs



## Assignment Project Exam Help

